

# Dependence of Diode's Behaviour on Conduction Time

## 1. Purpose:

In designing a power electronics system employing IGBT modules, the reverse recovery energy loss  $E_{rr}$  of a freewheeling diode is one of essential items which should be evaluated. The value of the energy loss increases with the diode conduction time and reaches a saturation state. Therefore, the value must be measured with a sufficiently long conduction time. The aforementioned saturation characteristics are also true of a stored charge ( $Q_{rr}$ ) and a reverse recovery current peak ( $I_{rm}$ ). In this application note the saturation characteristics of  $E_{rr}$ ,  $Q_{rr}$  and  $I_{rm}$  are reviewed as is a proper conduction time for evaluating diode behaviour.

## 2. Definition of conduction time $T_{co}$ :

In this section, the definition of the diode's conduction time is explained in connection with the operation waveforms of a half-bridge circuit. Fig. 1 shows the half-bridge circuit generally used for measuring the dynamic characteristics of power devices. The reverse recovery waveforms of a freewheeling diode are measured by operating the half-bridge circuit under the gate voltage pattern of Fig. 2(a). The voltage and current waveforms are schematically shown in Fig. 2(b) and (c) respectively. In accordance with the gate pattern, IGBT B2, i.e. Module 2, is driven. From  $t = 0$  to  $t_1$  the state of B2 is ON and current  $I_C$  flows through load L and IGBT B2, as shown in Fig.3. In this case the load current  $I_L$ , which flows through an inductive load L, has the same value as the collector current  $I_C$  of B2, where  $I_C$  increases with time. After  $t_1$ , B2 shifts to OFF-state through a transient period. During the OFF-state of B2,

the current  $I_C$  is blocked but the load current  $I_L$  is maintained as a circulating current through diode D1 as shown in Fig.4. After  $t_2$ , B2 is turned on again during a transient period. Just after  $t_1$  and  $t_2$ , a transient state occurs, where both  $I_C$  and  $I_L$  flow as shown in Fig.5. The reverse current  $I_R$  of D1 is the difference between  $I_C$  and  $I_L$ , that is,  $I_R = I_C - I_L$ . The conduction time is defined as the period  $T_{CO}$  in Fig. 2(c) where the forward current, that is a negative value of  $I_R$ , flows through the diode.

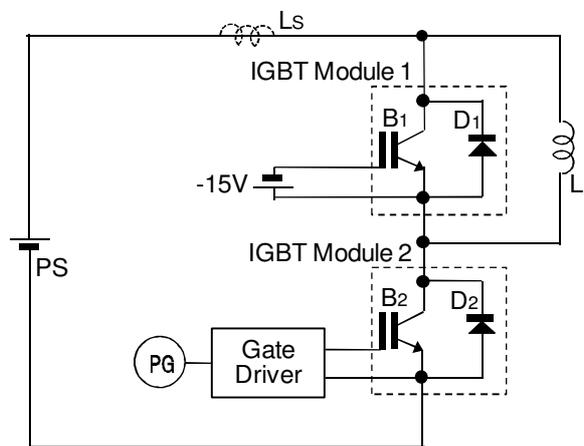


Fig.1 Half-bridge circuit

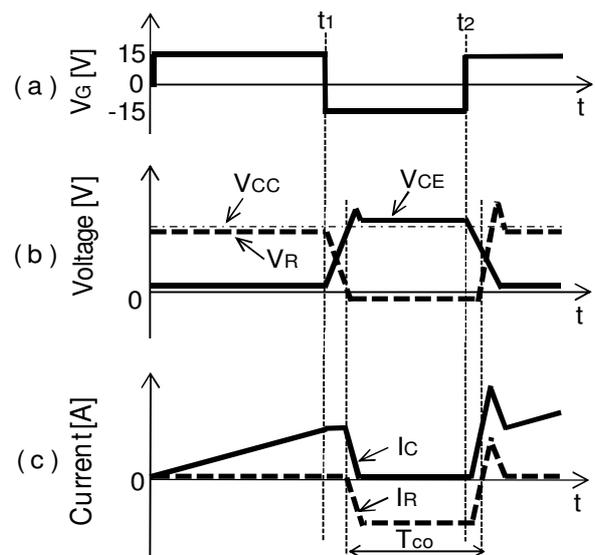


Fig.2 Operation pattern for B2

(Solid line: Waveform of B2, Dashed line Waveform of D1)

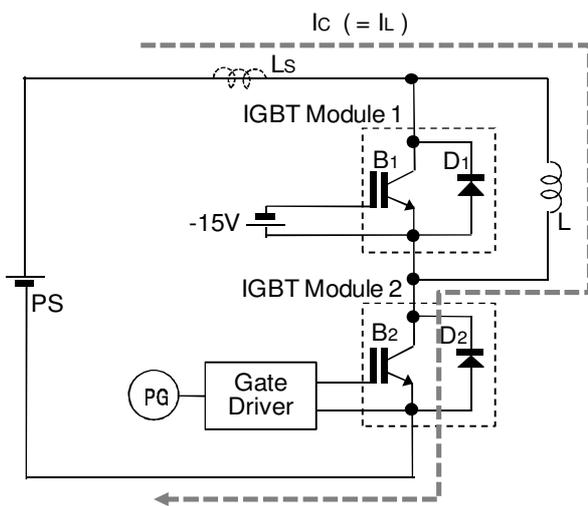


Fig.3 Current flow in ON-state of B2

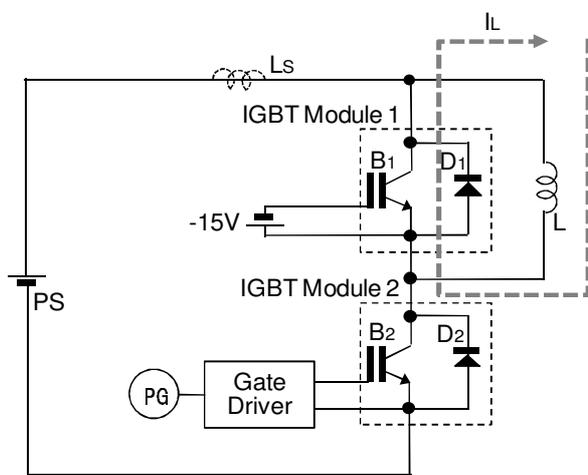


Fig.4 Current flow in OFF-state of B2

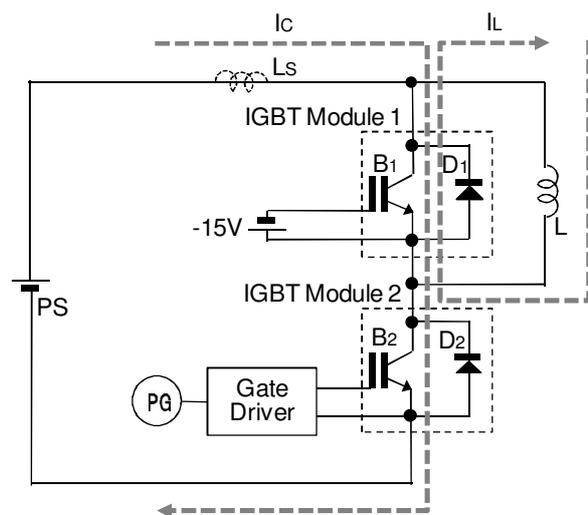


Fig.5 Current flow during transient period

### 3. Saturation characteristics of Err, Qrr and Irm:

The values of Err, Qrr and Irm rise with the increase of conduction time and reach a saturation state. The saturation characteristics of Err, Qrr and Irm can be experimentally verified using the half-bridge circuit. As a representative example, the diode's characteristics of the IGBT module MBN1200H45E2 are shown in Fig. 6, Fig. 7 and Fig. 8. The measuring conditions of the characteristics are as follows.

Measuring conditions:

- Supply voltage  $V_{cc} = 2600 \text{ V}$
- Forward current  $I_F = 1200 \text{ A}$
- Junction temperature =  $25^\circ\text{C}$  and  $125^\circ\text{C}$
- Stray inductance  $L_s = 150\text{nH}$
- Gate resistance =  $3.3\Omega$

Fig. 6 shows the characteristics of the reverse recovery energy loss Err at diode junction temperature  $25^\circ\text{C}$  and  $125^\circ\text{C}$ . In the case of the junction temperature  $25^\circ\text{C}$ , the characteristics curve is saturated in the domain where the conduction time is over  $40\mu\text{s}$ . Where the junction temperature is  $125^\circ\text{C}$ ; the curve reaches a saturation state after approximately  $60\mu\text{s}$  conduction period. Figures 7 and 8 show the characteristics of Qrr and Irm respectively, where both characteristics curves of Qrr and Irm are saturated after the same conduction time of Err.

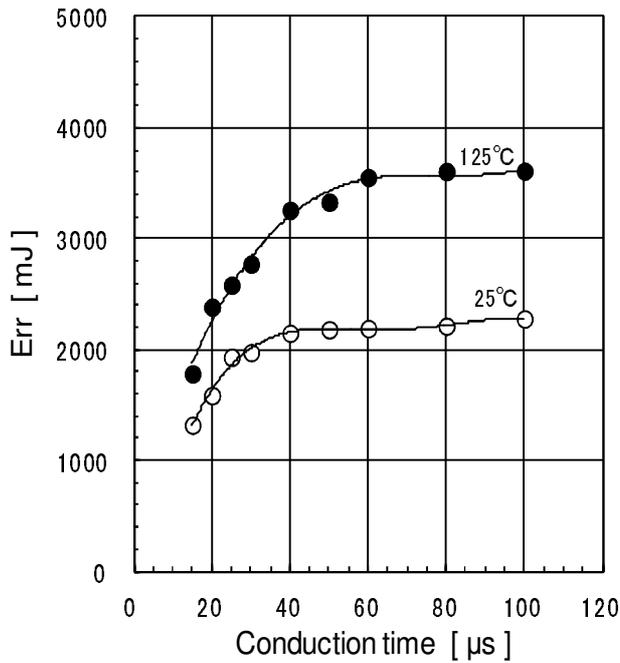


Fig. 6 Dependence of Err on conduction time

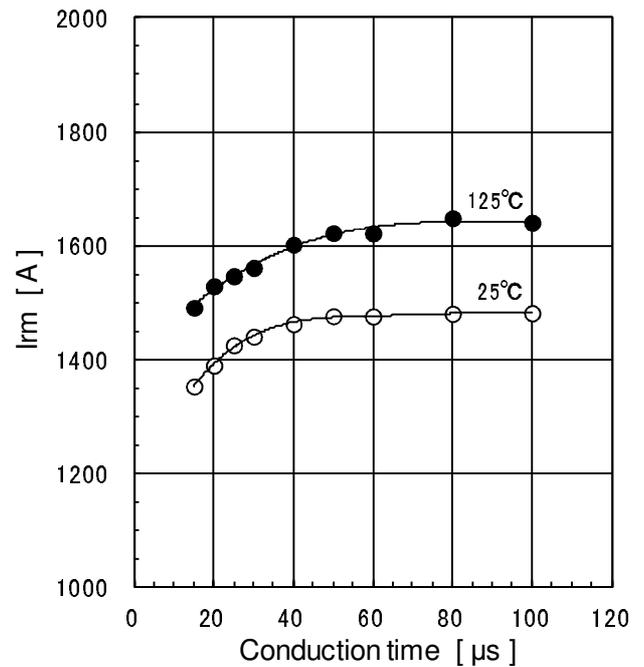


Fig. 8 Dependence of Irm on conduction time

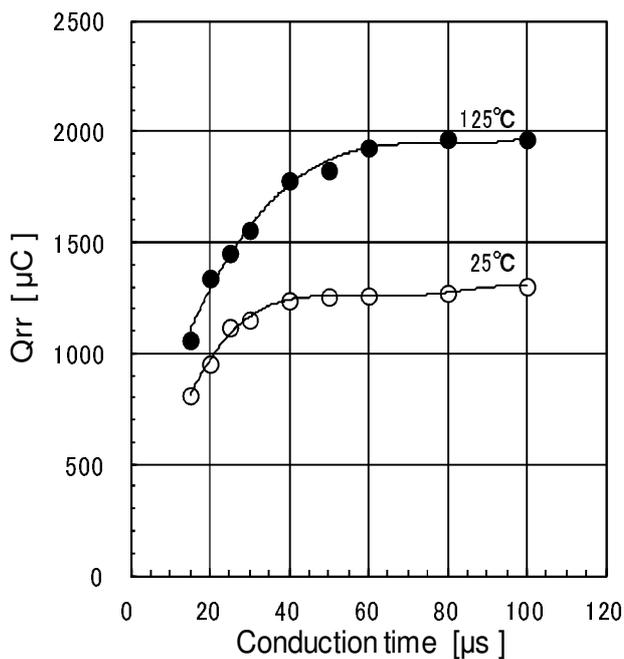


Fig. 7 Dependence of Qrr on conduction time

#### 4. Proper conduction time:

As mentioned in the preceding section, Err, Qrr and Irm exhibit saturation characteristics with an increase of diode conduction time. Therefore, in evaluating a diode's behaviour, a sufficient conduction time must be ensured to avoid the influence of the diode's transient characteristics. In this document the behaviour of a diode was the focus, however an IGBT also exhibits a similar saturation tendency. Therefore, when evaluating the turn-on and turn-off power loss of an IGBT, a suitable value of conduction time must be considered.